

This question paper contains 2 printed pages]

GA—118—2023

FACULTY OF SCIENCE

B.Sc. (First Year) (Second Semester) EXAMINATION

APRIL/MAY, 2023

(New Course)

ELECTRONICS

Paper III

(Semiconductor Devices and Electronic Instruments)

(Thursday, 11-5-2023)

Time : 10.00 a.m. to 12.00 noon

Time—Two Hours

Maximum Marks—40

N.B. :- (i) Attempt All questions.

(ii) Illustrate your answer with suitable labelled diagrams wherever necessary

1. Explain construction, working and characteristics of Light Emitting Diode (LED) with suitable diagram. 15

Or

(a) Explain construction of NPN and PNP transistor with neat diagram. 8

(b) Explain characteristics of UJT. 7

2. Explain construction and working of full-wave rectifier. Also derive the expression for average value and efficiency. 15

Or

(a) Explain application of CRO. 8

(b) Explain how you will convert a galvanometer into ammeter. 7

P.T.O.

3. Explain any *two* of the following :

10

- (a) Photodiode
- (b) α_{dc} and β_{dc} of a transistor
- (c) Bridge rectifier
- (d) Various controls of CRO.

<https://www.srtmunonline.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से