

This question paper contains 4 printed pages]

**R—126—2017**

**FACULTY OF SCIENCE**

**B.Sc. (Fourth Semester) EXAMINATION**

**MARCH/APRIL, 2017**

**PHYSICS**

**Paper IX**

**(Basic Electronics)**

**(MCQ+Theory)**

**(Tuesday, 11-4-2017)**

**Time : 2.00 p.m. to 4.00 p.m.**

*Time—2 Hours*

*Maximum Marks—40*

*N.B. :— (i) All questions are compulsory.*

*(ii) First 30 minutes are for question no. 1 (MCQ) and remaining time is for other questions.*

*(iii) Figures to the right indicate full marks.*

*(iv) Use black ball point pen to darken the circle of correct choice in OMR answer-sheet.*

**(MCQs)**

1. Choose the *correct* answer : 10

(i) The line regulation indicates .....

(a) Change in output voltage due to change in input voltage

(b) Change in output voltage due to change in input current

(c) Change in output voltage due to change in load current

(d) None of the above

(ii) A Zener regulator ..... in the power supply.

(a) Increases the ripple

(b) Data insufficient

(c) Decreases the ripple

(d) Neither increases nor decreases the ripple

P.T.O.

- (iii) The voltage gain of a transistor connected in common collector arrangement is .....
- (a) equal to 1                      (b) more than 10  
(c) more than 100                (d) less than 1
- (iv) A transistor is connected in CB mode. If it is now connected in CE mode with same bias voltage, the values of  $I_E$ ,  $I_B$  and  $I_C$  will .....
- (a) remain the same                (b) increase  
(c) decrease                        (d) become zero
- (v) The op-amp can amplify .....
- (a) a.c. signals only  
(b) d.c. signals only  
(c) both a.c. and d.c. signals  
(d) neither d.c. nor a.c. signals
- (vi) The input impedance of a differential amplifier equals  $r_e'$  times .....
- (a)  $\beta$                                 (b)  $R_E$   
(c)  $R_C$                               (d)  $2\beta$
- (vii) In an LC oscillator, if the value of L is increased four times, the frequency of oscillations is .....
- (a) increased 2 times  
(b) decreased 4 times  
(c) increased 4 times  
(d) decreased 2 times
- (viii) An oscillator produces ..... oscillations.
- (a) damped                        (b) undamped  
(c) modulated                    (d) unmodulated

(ix) In LC oscillators, the frequency of oscillations is given by .....

- |                               |                                |
|-------------------------------|--------------------------------|
| (a) $\frac{2\pi}{\sqrt{LC}}$  | (b) $\frac{\sqrt{LC}}{2\pi}$   |
| (c) $\frac{1}{2\pi\sqrt{LC}}$ | (d) $\frac{2\pi L}{\sqrt{LC}}$ |

(x) The minimum load resistance is given by .....

- |                             |                             |
|-----------------------------|-----------------------------|
| (a) $\frac{V_{NL}}{I_{FL}}$ | (b) $\frac{V_{FL}}{I_{FL}}$ |
| (c) $\frac{V_{NL}}{I_{FL}}$ | (d) $\frac{V_{NL}}{I_{NL}}$ |

**(Theory)**

2. Attempt any *five* : 10

- (a) If the d.c. output voltage is 400 V with no-load attached to power supply but decreases to 300 V at full-load, find the percentage voltage regulation.
- (b) Draw a well labelled diagram of CE connections.
- (c) Define slew rate in operational amplifier.
- (d) Give the expression for frequency of oscillations in Colpitt's oscillator.
- (e) Define load regulation.
- (f) Define input bias current in op-amp.
- (g) What is Barkhausen criterion in oscillator ?

3. Attempt any *two* : 10

- (a) Explain Zener-diode voltage regulator with neat diagram.
- (b) Determine the output characteristics of CB connections.

P.T.O.

- (c) Write a note on inverting amplifier in an op-amp.
- (d) Explain the action of phase shift oscillator with neat labelled diagram.
4. Attempt the following questions :
- (a) Explain the working of a transistor series voltage regulator d.c. power supply. 5
- (b) Write a note on operating point on a d.c. load line. 5
- Or*
- (x) Discuss the operation of a differential amplifier. 5
- (y) Discuss the essentials of a sinusoidal oscillator. 5